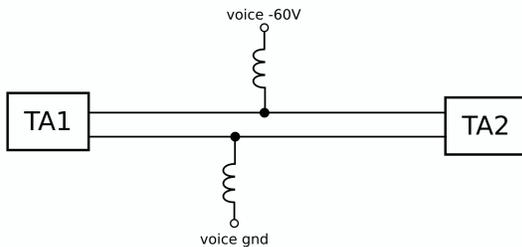


## Connecting Two Phones


A simple two-way phone line may be built like this:



Coils are actually part of a relay. A special telephone relay with two coils and a single anchor can be used, but for now, it's okay to use two separate 24V relays. T coils pass direct current to power the phones, but resist alternating voice current and force it to go through another phone, rather than back through the power supply.

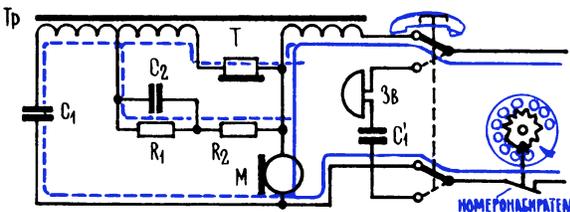
## Ringling the Phone

Here is a simplified schematic of an old landline phone.




The phone does not pass direct current while on-hook, but it does pass alternating ring current. The ring capacitor value is typically  $1\mu F @ 250V$ . Some old phones have ring and voice capacitors made as a single unit, like the one shown here, but they are two separate capacitors anyway. So we need to apply al-

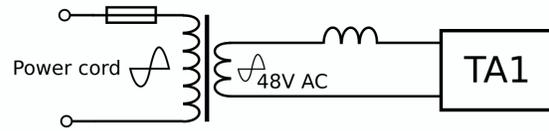ternating current to the phone in order to make it ring, as in this design where a relay coil is used to decrease the ring voltage a little.



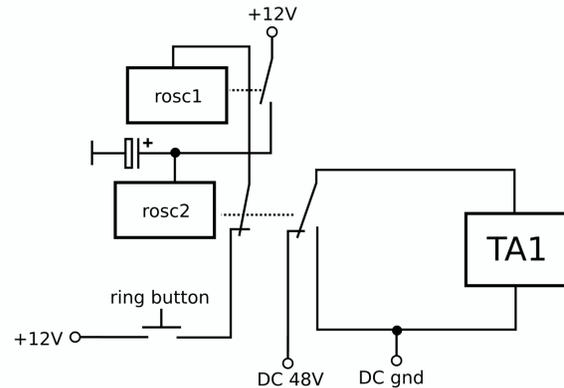Another way to generate ring current is to use a pulse pair of two relays, like this:



A phone handset shouldn't be lifted during the ring cycle, as the voice circuit on newer phones can be damaged by the ring current. I blew up one of my phones this way. Also, direct voltage must be mixed with alternating voltage, it is required for some phones to operate correctly.


A more sophisticated schematic is shown in Figure 8, with the marked region discussed extensively here. A single relay with two coils A1 and A2 is used to power the phone. One coil can be shorted to make relay operate slower. This relay ignores ring current, but will detect off-hook direct current and disable ring. Busy relay RB is used to detect long (on-hook) pulse from the phone and perform reset.

An additional coil of power transformer is used to mix  $-60V$  with 50/60 Hz 48V ring voltage. 50 Hz is a little fast for the phone, but still acceptable. Normal ring speed would be 25 Hz or so.


The positive power pole may be connected to ground, this will decrease corrosion on wires though an effect called cathodic protection, especially when an underground line is used. Unlike switching-mode power supplies, a power transformer galvanically separates the line from the mains network.

You might wonder why 48 VAC becomes 60 VDC

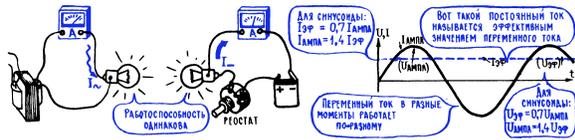
after the rectifier? That's because AC voltage is measured in RMS value. Peak voltage values can be derived from RMS when needed.



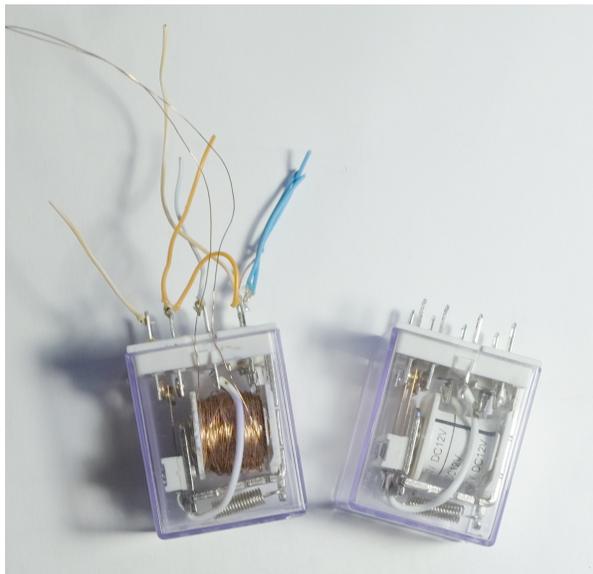A normal single-coil relay can be modified to accommodate a second coil, simply by winding another coil up on top of factory coil, like this.



## Two-way Phone Line with Ring

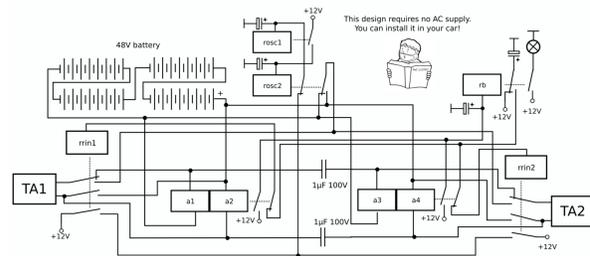

In this design, relays A1 to A4 are separate 24V relays without shared coils. The other five are 12V logic relays. 48V DC can be drawn from four 12V lead-acid batteries, or from some other source.  $1\mu F$  capacitors divide the voice line into two independently controllable parts. The busy relay RB is shared between two phones. When one phone goes off-hook, a ring cycle will be triggered in the on-hook phone. The ring length is set by the value of the upper capacitor near the RB relay. This simple design is recommended for home use, as it requires little debugging effort.

## Manual Switching

Almost all early manual telephone exchanges, both large and small, have parts in common. For each telephone there will be numbered socket on the board accompanied by line indication lamps. PBX operators would use connection kits to talk with customers and perform connections to other phones or trunks. Each connection kit has two wires with stan-


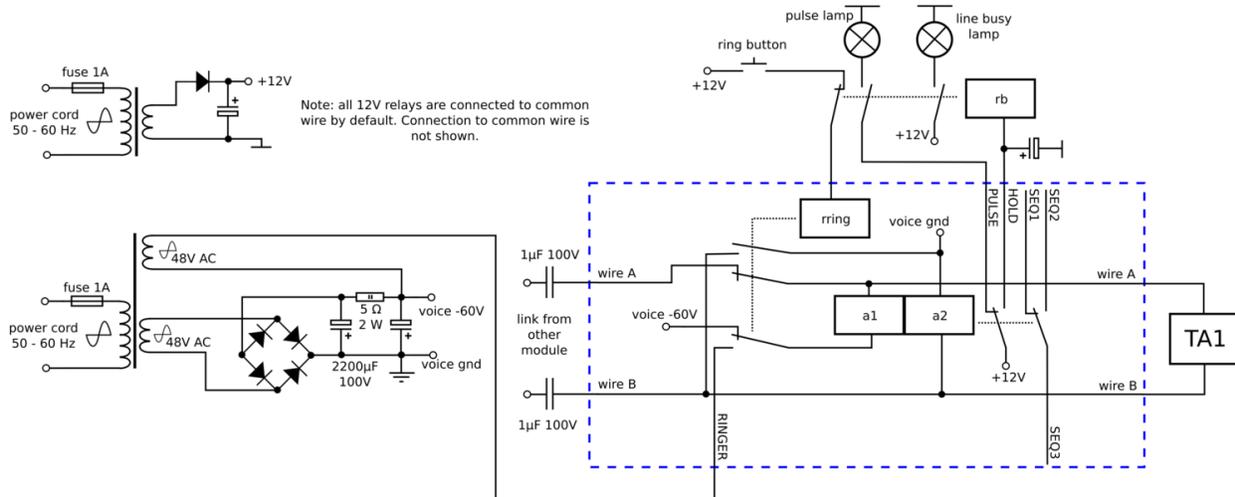


Figure 8: A more sophisticated phone schematic.

standard 3-pole TT jacks at the end. Each wire has a corresponding tri-state switch for sending ring signals and for connecting an operator's headset to the phone.

Trunk lines are used to route call between exchanges. Customers were not allowed to talk to other exchange operator via trunk lines, it's the operators who would have to talk to one another via the trunk to setup calls.

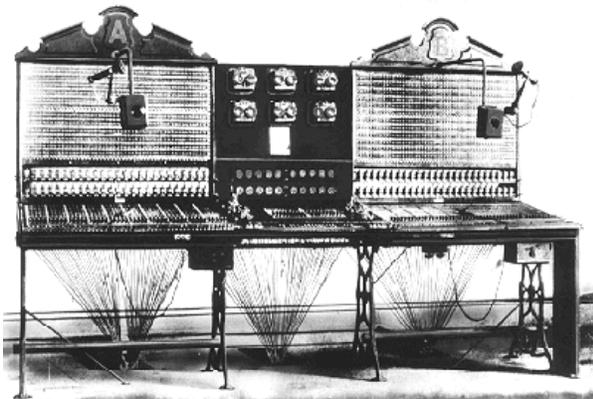Manual exchanges have poor scalability. One improvement was to implement an exchange with separate panels, A and B. The operator at panel A would ask the customer about the destination number, while the operator at panel B would perform the connection to the destination phone.



<sup>13</sup><http://library.lol/main/bbe9fc9ddf1be20fc491e8e4b997da70>


<sup>14</sup><http://library.lol/main/321ac6b297bd75792f318fed8da5928e>


## Automatic Step-by-Step Switching

I need to make a note about terminology. I have two reference books on my mind: first is a Soviet ATS-47 reference book,<sup>13</sup> and the second is AT&T's training course.<sup>14</sup> There is no strict terminology in this article, but I'm going to use the terms "forward seeking" and "backward seeking" from ATS-47 to explain one thing.


Each phone line usually has some fixed amount of equipment at the exchange office, a so called "line kit." For 10,000 phone lines there will be 10,000 line kits. Yes, sometimes two phones may be connected to one phone line and share a line kit. (Only one phone may be active, depending on polarity.) The line kit will activate other equipment when a customer begins the call. The line kit must be relatively small, especially for a home-made telephone exchange.

The Soviet ATS-47 setup uses forward seeking at the call pre-setup stage. This means that each line kit has a stepping switch which selects a free line for next dialing stage. After the call, it must return back to the home position to accept more incoming calls. Up to ten group-seekers can be connected to the outputs. This works faster than the backward seeking method, but it requires one rotating one-motion switch to be in each line kit, which can be expensive.

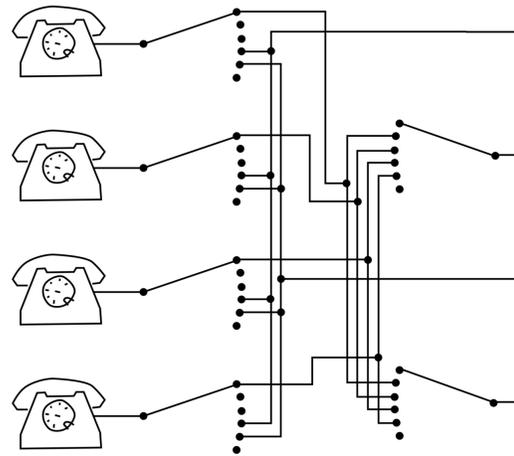

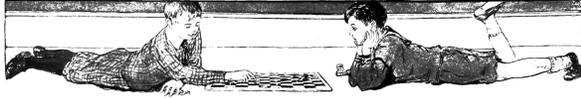

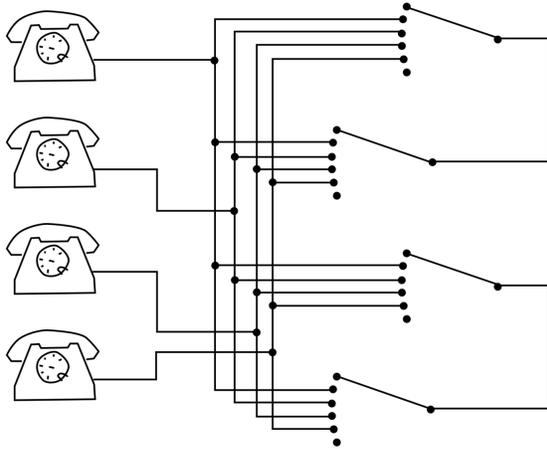Backward seeking is more like manual switching. The kit consists of two switches, with the first switch (the line hunter) navigating to the phone that needs to be served. The second switch accepts one digit and connects to the destination phone.



Switch operation may be driven by pulses coming from the phone, which is slow, or it may be free switching, where the switch quickly steps itself until it finds the right position.

### Strowger Switches and Trunk Lines


It's a good idea to use a Strowger switch with 100 outputs as an output switch. It will consume the two final digits of the phone number to drive its arm up and then around to the desired contact.

If we have more than 100 phones we'll use group seeking. A group seeker is a Strowger switch that accepts one digit to drive the arm up, and then seeks a free device from the next stage to continue dialing. Up to ten devices may be connected to the digit. If no free device is found, the arm will stop at the "trunk busy" contact at the end of the row. The group seeker must find the free line before more digit pulses begin to arrive, so all but the very oldest exchanges have a special mechanical feature to increase the pause between digits.

The line hunter is a Strowger switch, too. It connects one of the phones to the first stage group seeker. A dial tone in the handset means that first stage seeker is waiting for its first digit. A special

device is used to prevent multiple seekers from hunting the same phone. When all line hunters are busy, there will be no dial tone heard. Hot line phones, such as street phones and PBX trunks, may be connected to the first stage directly without the pre-setup stage, such phone will have one dedicated first stage device.

Wires A and B are used for voice and pulses transfer and for reset signaling between group seekers. Wire C is used to mark the line as free or busy. Most Strowger switches have three arrays of outputs and three contact arms, sometimes two fields are sufficient.

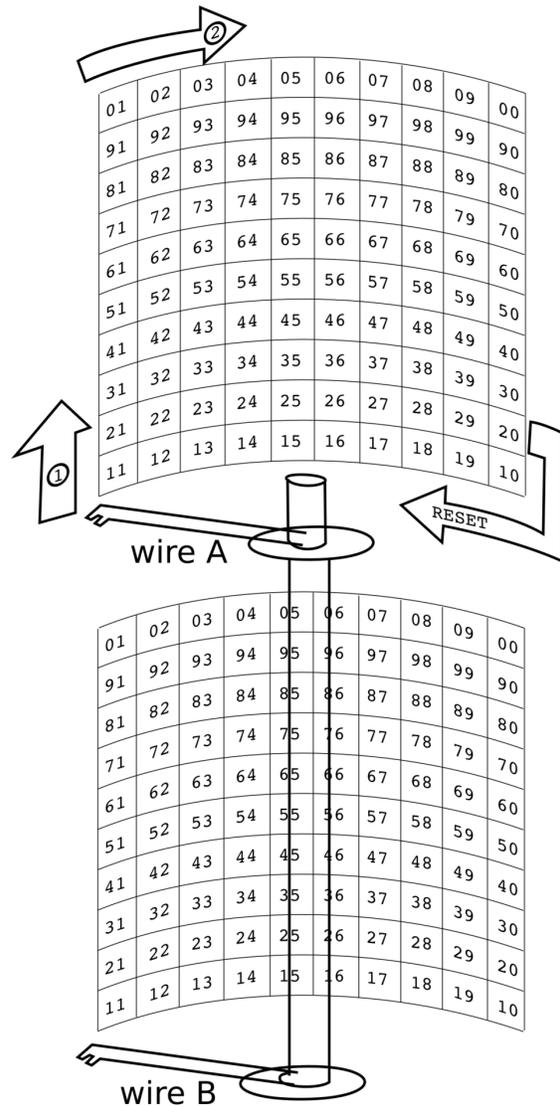

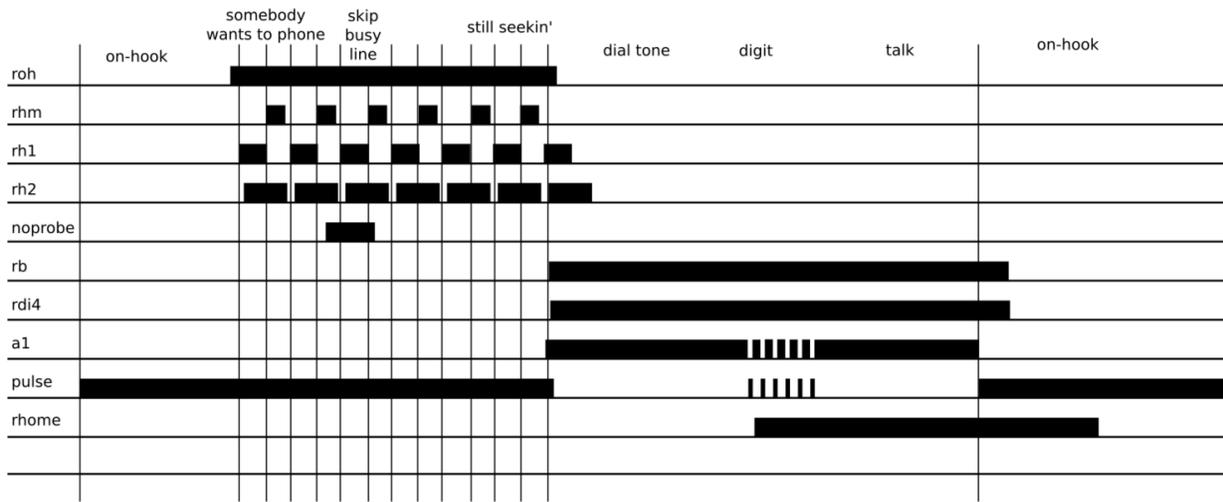


Figure 9: First Timing Diagram


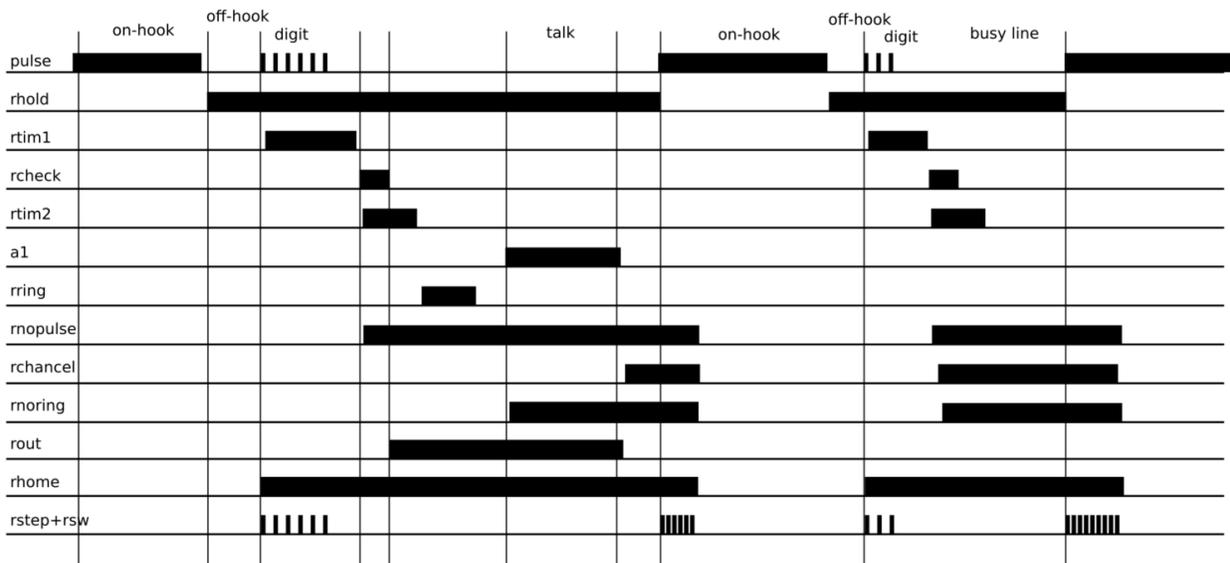


Figure 10: Second Timing Diagram

## PoC Telephone Exchange Unit

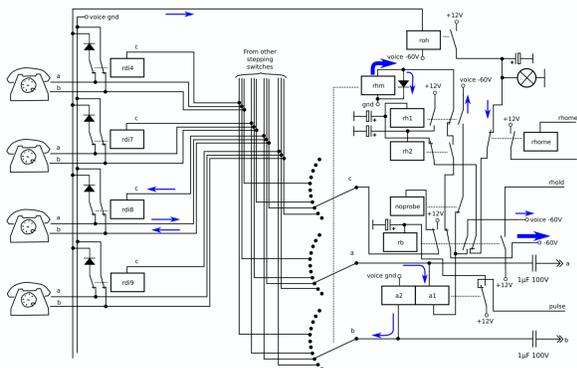

I'm going to show you a more complicated design, one that I've built. It has just two rotating switches, so only one pair of telephones may use the connection kit, and other telephones must wait their turn. Up to ten phones may be used total. There is no dial tone circuit, as that would require an additional coil on the A1-A2 relay.

**All About**

# OSI

**BASIC-IN-ROM**

Ohio Scientific Microsoft BASIC Ver 1.0 Rev 3.2  
REFERENCE MANUAL

*Complete, Concise, Accurate, Detailed. All  
commands, statements, and functions. Maps.  
USR. Tapes. Bug fixes. Variable tables.  
Source code storage. MONITOR.*


Postpaid \$8.95. Send check, or COD

**EDWARD H. CARLSON**    259  
3872 RALEIGH DR.  
OKEMOS, MI 48864

Dealer Inquiries Welcome

In real-world systems, wire C is more complicated. One simplification was to use HIGH (12V) logic level on wire C as a busy signal, to keep the line kits small. Here every line kit contains one relay and one diode. (An optional indication bulb may be hooked to wire C.) This design can be joined with a manual exchange desk, provided that each socket will pull C high to prevent the line from automatic switching.

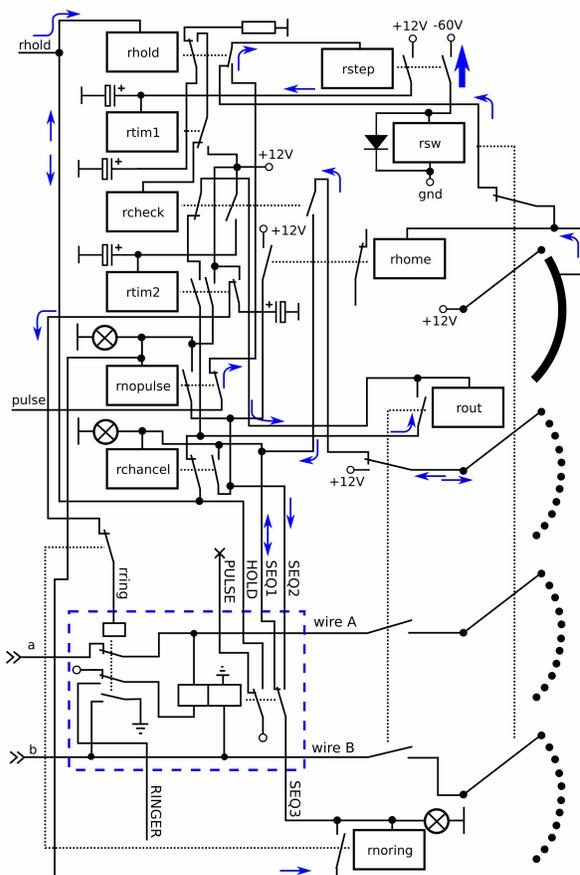ROH is an off-hook detection relay, it has 48V coil. The A1, A2 relays have 24V coils. All others are 12V logic relays with the other pole connected to logic ground. Some of them have capacitors to increase release time. Figure 9 is a timing diagram that will help you understand the logic.




RHM and RSW are stepping relay magnets. They draw current up to 1A, so protection diodes are there to reduce sparks on relay contacts. Both stepping relay and phones draw power from the same power transformer, but there are two diode bridges, one for voice circuit and one for the magnets. Without that, the RSW relay would cause brownouts on the  $-60\text{V}$  supply and the phone would be unable to send clear pulses. The second part of the circuit performs the line checking sequence. diagram for second part: This second timing diagram is shown in Figure 10.

### What are values of those capacitors?

Capacitors are used here to increase relay release time. When a relay is powered, the capacitor charges itself and accumulates a bit of energy. After power removal, the capacitor will power the relay for two seconds or so, and then discharge. The resulting delay time depends on the relay armature type, capacitor value and other things.


A  $1000\mu\text{F}$  capacitor with 12V relay coil will give 200 milliseconds delay or so. It's suitable for the RB, RTIM1, RTIM2, RCHECK relays.  $100\mu\text{F}$  is good for fast processes, like line hunters RH1 and RH2.  $3300\mu\text{F}$  will power the RRING relay, giving 600 milliseconds of ringing.

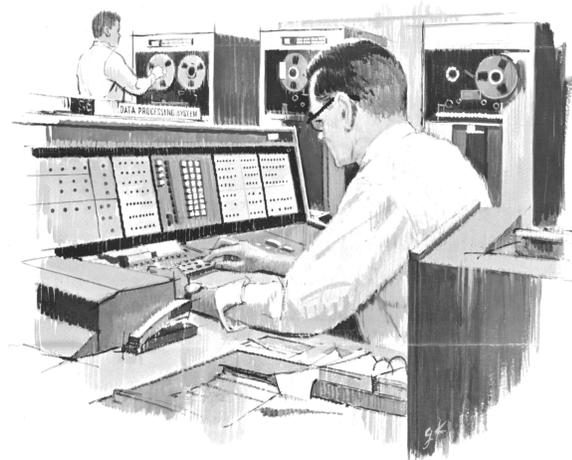An alternative way to slow down a relay is to short-circuit one of its coils or add a copper disc near the coil. This increases the inductance of the relay, and therefore also its release time.



<sup>15</sup>unzip pocorgtfo21.pdf phones3.mp3

### How to protect relay contacts?

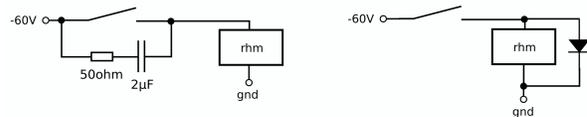

Inductive loads like relay coils, large electromagnets, and DC motors will generate inductive peak voltage when disconnected. This inductive current will generate sparks and degrade switching contacts that control inductive circuit, so a protection diode is needed.

ATS-47 uses RC filters instead. Spark current can have high frequency components, and the filter will pass it around and decrease interference to other equipment. It's okay to use both diodes and RC-filters, of course.

### Audio!

I've made a small audio recording.<sup>15</sup> Listening to it, you can hear my telephone exchange unit in action. Various phone rings and rotary dial sounds follow starting from 0:37. The ring sound will differ depending on buzzer current frequency, I've tried both fast (50Hz) and slow (using relays).

### How can we trace a call?

On the ATS-47 all switches used in a call cannot be released until the recipient phone goes back on its hook. This can be used to track the originating phone, even if the caller has gone back on the hook.

Having received a call, the recipient might dial a special digit to signal an operator, who can then be asked to track the circuit back to the originating phone. During this time, the caller is unable to make another outbound call.


Wires A and B between switches are used to transfer signals about answered phone and reset, along the voice. These signals activate the successful calls counter, which is used for billing. A first stage seeker may swap the originating phone line polarity when the other phone is answered. Manual exchanges use this as an additional indication that recipient is ready to talk. Street phones will grab the coin when the line polarity is reversed.

A customer often forgets to place his handset on-hook. There is a special circuit to detect such phones, with a delay of one or two minutes.
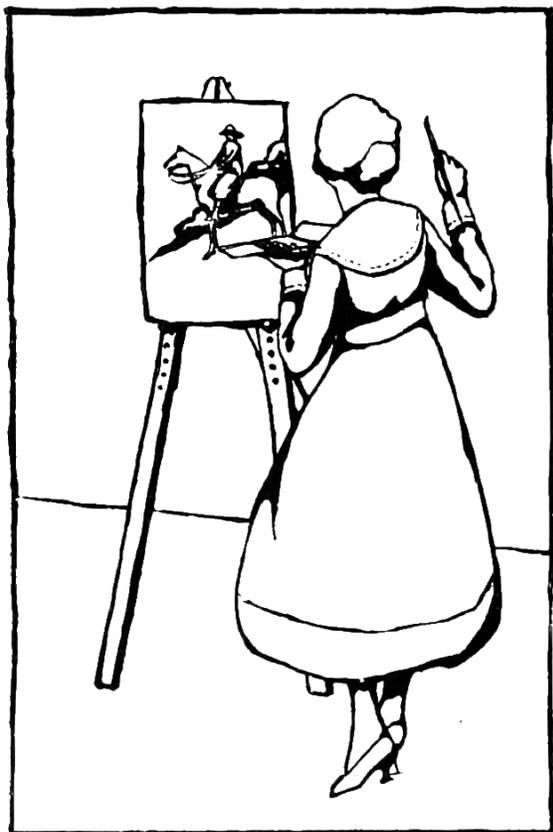
## Greetings for the neighbors!

I'm not alone in building relay-based devices. In fact, there is whole Hackaday thread about this.<sup>16</sup> There's also Artyom Kashcanov aka Radiolok (Hi!) and his *BrainfuckPC*.

There is Harry Porter and his *HPRC*; Harry made a very nice introductory video about relay logic.<sup>17</sup> And Michael whose demonstration setup using five Strowger switches is well documented at his homepage.<sup>18</sup> Em Lazer-Walker uses small PBX switchboard as a front-end for her videogame. Frankfurt's Museum of Communication also has a large working demonstration setup.



1	Exxon
2	General Motors
3	Mobil
4	Ford Motor
5	IBM
6	Texaco
7	E.I. du Pont
8	Standard Oil (Ind.)
9	Standard Oil of Cal.
10	General Electric
11	Gulf Oil
12	Atlantic Richfield
13	Shell Oil
14	Occidental Petroleum
15	U.S. Steel
16	Phillips Petroleum
17	Sup

**27  
million  
Americans  
can't read.  
And guess  
who pays  
the price.**

Every year, functional illiteracy costs American business billions.

But your company can fight back...by joining your local community's fight against illiteracy. Call the Coalition for Literacy at toll-free **1-800-228-8813** and find out how.

You may find it's the greatest cost-saving measure your company has ever taken.

**A literate  
America is a  
good investment.**

**Ad  
Council**  Coalition for Literacy



**Softstrip**


<sup>16</sup><https://hackaday.io/project/11798-relay-based-projects>

<sup>17</sup><http://web.cecs.pdx.edu/~harry/Relay/VideoTutorial/index.html>


<sup>18</sup><https://www.seg.co.uk/telecomm/automat4.htm>

# Do-It-Yourself: Stepping Telephone Exchange


## Lesson 1. Connect two phones:

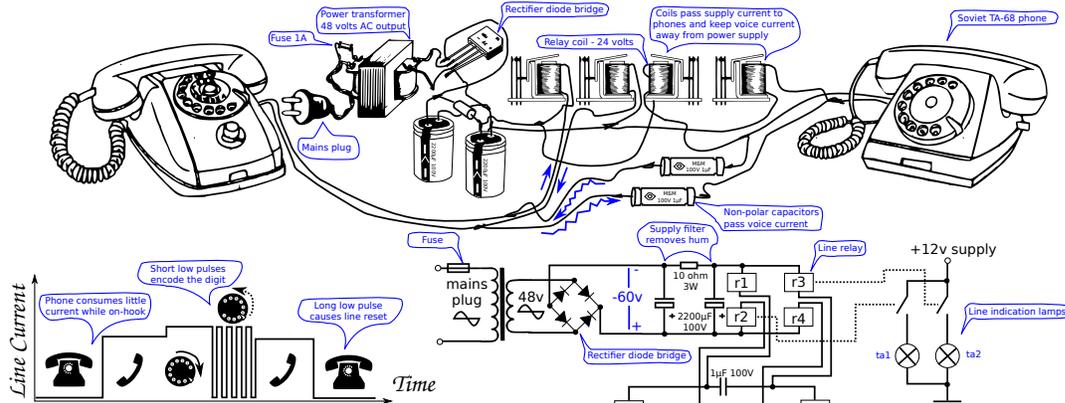


## Lesson 2. Ring the phone:

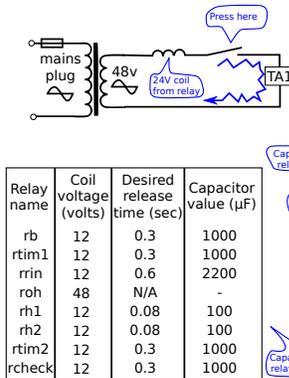
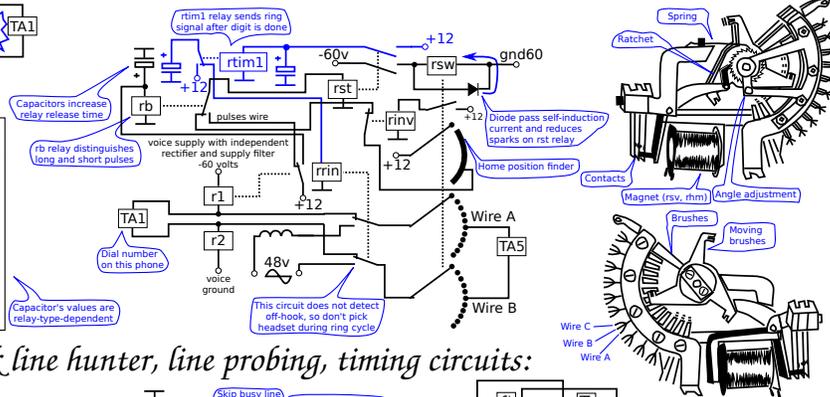
## Lesson 3. Connect phone to Stepping Switch (easy way):


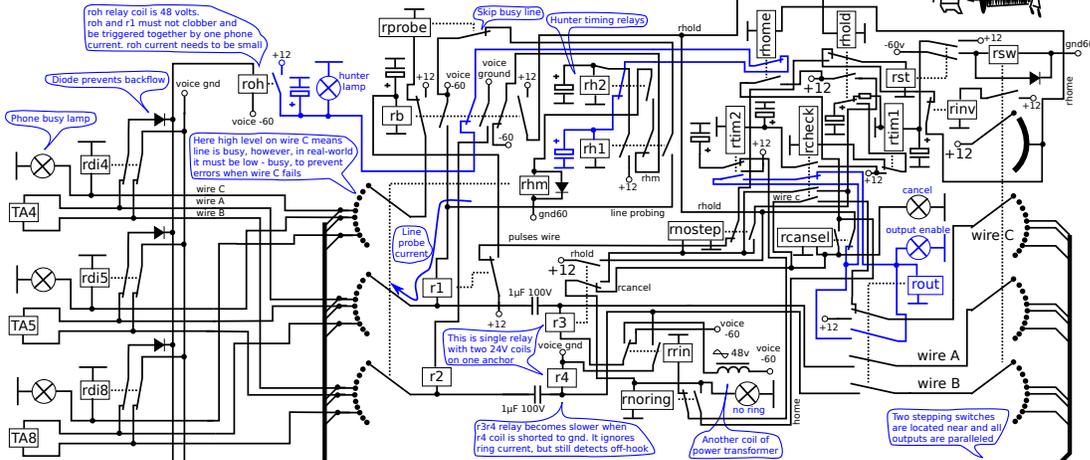
## Lesson 4. Off-hook line hunter, line probing, timing circuits:



See also: International Journal of Proof of Concept or GTFO issue 0x21, long article about phones

-> pagedout.institute <- issue #3 2020